

Lesson 3: Worksheet 2



 	•	4.1		
l it	ĦΥ	the	CITC	1117

Use each material to try and fix the circuit.

Does it work or not?

Can you work out a pattern?

You can try lots of different materials such as paper clips; ruler; rubber; small plastic ruler; teaspoon; elastic band; tin foil; feather; buttons; pencil; pencil sharpener; wool etc.

Ubject	Result			
•••••••				
think the pattern is:				